

EE2001 - Digital systems lab

Janakiraman Viraraghavan and Vinita Vasudevan



Verilog data, modules and Ports

Data Values:

- ▶ 0, 1, X (unknown), Z (tristate)
- ▶ $a[3:0] \implies a[0]$ is the LSB and $a[3]$ is the MSB

```
module Circuit(out1, out2, Inp1, Inp2);
    output out1, out2;
```

HDL Modelling of functionality

```
endmodule
```

```
module A(a, b, sum, cout);
    input[3:0] a, b;
    output[3:0] sum; output cout;
```

HDL Modelling of functionality

```
endmodule
```

Half Adder - Gate level and Data flow model

a	b	sum	cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- ▶ Gates and, or, not, xor, nand, nor, xnor predefined
- ▶ Bit operators similar to C
- ▶ The inputs a and b are in the “sensitivity list”. If there is any change in a or b, the corresponding output is re-evaluated.

Gate level Model

```
//Half adder module

module ha(a, b, sum, cout);

input a, b;
output sum, cout;

xor x1(sum, a, b);
and a1(cout, a, b);

endmodule
```

Data flow model of half adder:

```
//Half adder module

module ha(a, b, sum, cout);

input a, b;
output sum, cout;

assign sum = a ^ b;
assign cout = a & b;

endmodule
```

Full Adder Truth Table

a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{sum}(a, b, \text{cin}) = \Sigma(1, 2, 4, 7)$$

$$= a \oplus b \oplus \text{cin}$$

$$\text{cout}(a, b, \text{cin}) = \Sigma(3, 5, 6, 7)$$

$$= a b + b \text{ cin} + a \text{ cin}$$

Hierarchical modelling

A module can contain other modules through module instantiation.

- ▶ Modules are connected together using nets
- ▶ Ports are attached to nets either by position or name

```
module FA(ain , bin , carryin , sum , cout );


input ain , bin , carryin ;
output sum , cout ;
wire s1 , c1 , c2 ; These are nets connecting the half adders and OR gates

  ha ha1(.a(ain), .b(bin), .cout(c1), .sum(s1)); Bind to signals by name
  ha ha1(ain , bin , s1 , c1); // By position
  ha ha2( s1 , carryin , sum , c2 );
  or or1( cout , c1 , c2 );
  // assign cout = c1 | c2;
endmodule
```

Can interchange the order of the statements without affecting the output

Testbench

 - ▶ The testbench is also a module
- ▶ Data type called “reg”. Can assign values to variables that are declared as reg.
- ▶ Data format



- ▶ Declared as
`reg[3:0] a;`
`a = 4'b1010;`

```
//Half adder test bench
```

```
module test_ha;           //test bench module
  wire s, c;              //outputs from half adder
  reg a, b;                //inputs to the half adder module

  ha DUT(a, b, s, c);      //instantiate the device under test (half adder)

  initial
  begin
    $monitor(" At_t=%t, a=%b, b=%b, s=%b, c=%b", $time, a, b, s, c);
    a = 1; b = 1;          // t = 0
    #10 a = 1; b = 0;       //change values of a and b after 10 units of time
    #10 a = 0; b = 1;       // t = 20
    #10 a = 0; b = 0;

    #10 $finish;
  end
endmodule
```

Experiment 3: Multi-Bit data and Behavioural Test Bench

Objective: Build a multi-bit adder and verify the functionality across all input combinations.

- ▶ Build a full adder using
 - a. Gate-level modelling
 - b. Data-flow modelling

You should have two different files describing the circuit using various approaches and one file containing the testbench. Do not use half adders to build the full adder.

- ▶ Use the one-bit full adder to build an EIGHT bit adder and do a logic simulation to verify its functionality for all possible input combinations.

Experiment 3: Use of Multi-bit Multiplexers


Objective: Build a small ALU that performs 4 operations based on a 2 bit instruction $I[1 : 0]$. You may use behavioural models for all the operations here. The operations are:

$I[1]$	$I[0]$	Operation
0	0	AND
0	1	OR
1	0	XOR
1	1	ADDITION

Input: $A[7 : 0]$, $B[7 : 0]$, $I[1 : 0]$ Output: $Y[7 : 0]$, $COUT$

Functional Simulation: Behavioural Modelling

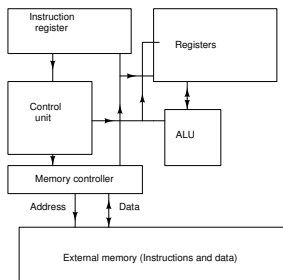
High level model specifying circuit function, without getting into actual implementation



Need to verify functionality/execution behaviour of various instructions, before going to gate level or even data flow level modelling. Easier to write a C programme to verify functionality, using loops, case statements etc.

Behavioural modelling also useful for components.

Example: Multiplexer

 

$$Out = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

C program

```

if (!S0 && !S1)
{
    Out = I0
}
else if (!S0 && S1)
{
    Out = I1
}
else if (S0 && !S1)
{
    Out = I2
}
else
{
    Out = I3
}
    
```

Data flow modelling using Verilog

```
module mux4( l0, l1, l2, l3, s, out );
```

```
input l0, l1, l2, l3 ;  
input[1:0] s;  
output out  
wire t0, t1;
```

```
assign t0 = (~s[1] & l0) | (s[1] & l2);  
assign t1 = (~s[1] & l1) | (s[1] & l3);  
assign out = (~s[0] & t0) | (s[0] & t1);
```

```
endmodule
```

```
module mux4( l0, l1, l2, l3, s, out );
```

```
input l0, l1, l2, l3 ;  
input[1:0] s;  
output out;
```

```
assign out = (s == 0)? l0:  
              (s == 1)? l1:  
              (s == 2)? l2:  
              (s == 3)? l3: 1'bx;
```

```
endmodule
```

Behavioural Modelling

```

module mux4(  l0, l1, l2, l3, s, out );

input l0, l1, l2, l3 ;
input[1:0] s;
output out;
reg out;

always@(l0 or l1 or l2 or l3 or s)
begin
  if (s == 0)
    out = l0;
  else if (s == 1)
    out = l1;
  else if (s == 2)
    out = l2;
  else if (s == 3)
    out = l3;
end

endmodule

```

- ▶ Code is similar to C
- ▶ The arguments to the always block constitute the sensitivity list. Any change in these inputs will cause the always block to execute
- ▶ The statements within the always block are executed sequentially
- ▶ In order to assign values to it, “out” has to be declared as “reg” (similar to what we did in test benches).

Can mix models

```
module circuit(  $l_0, l_1, l_2, l_3$ , s, a, b, c, d);
```

```
input  $l_0, l_1, l_2, l_3$  ;
```

```
input a, b;
```

```
input[1:0] s;
```

```
output c, d;
```

```
reg out;
```

```
always@( $l_0$  or  $l_1$  or  $l_2$  or  $l_3$  or s)
```

```
begin
```

```
case( s )
```

```
0: out =  $l_0$ ;
```

```
1: out =  $l_1$ ;
```

```
2: out =  $l_2$ ;
```


```
3: out =  $l_3$ ;
```

```
end
```

```
assign c = out & a;
```

```
xor x1(d, out, b);
```

```
endmodule
```

 

BACK UP SLIDES

Experiment 3: Behavioural modelling using Verilog

Objective: Model circuits using behavioural models.

- ▶ Try out the behavioural and data flow model of a 4-to-1 MUX.
- ▶ Model a 1-to-4 demultiplexer using a behavioural model.
- ▶ Repeat the experiment using a data-flow model model.
- ▶ A and B are 4-bit inputs and the output of the circuit is $MAX(A, B)$. You can use a mix of data flow and behavioural models if you wish.

In all three cases, write a test bench to test the circuit.

2s complement

- ▶ The decimal value of a n -bit binary number is $\sum_{i=0}^{n-1} a_i 2^i$.
- ▶ If a negative number is represented in the two's complement form, its decimal value is $-(2^n - \sum_{i=0}^{n-1} a_i 2^i)$.
- ▶ In practice it is obtained by first subtracting the number from $2^n - 1$ (each bit is complemented) and then adding 1 to the number.
- ▶ For a positive number $a_{n-1} = 0$ and for a negative number $a_{n-1} = 1$.

- ▶ Positive number the decimal value is $\sum_{i=0}^{n-2} a_i 2^i$. Negative

$$\text{number: } -(2^n - 2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i) = -2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

2s complement

- ▶ In general, the value is $-a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$
- ▶ if A is an n bit number $a_{n-1}a_{n-2} \cdots a_0$, we need $A - A = 0$. If the sum is also n bits, throw away the carry out from the MSB
- ▶ If the sum is $n + 1$ bits? Do a sign extension. Verify that the decimal value of the number does not change with sign extension.
- ▶ How do you deal with fractions?